

The Siemens logo consists of a large square with a blue-to-green gradient. The word "SIEMENS" is centered within this square in a white, bold, sans-serif font.

SIEMENS

LAB-6

1. Your Verilog-A model for the PFD.

```
// AMS PLL Project: Phase Frequency Detector (PFD)

`include "constants.vams"
`include "disciplines.vams"

// REF: Reference signal
// FB: Feedback signal
// UP: Up signal (FB late)
// DN: Down signal (FB early)
module PFD2(REF,FB,UP,DN);
    // VDD and threshold voltage for digital signals
    parameter real VDD = 1.2;
    parameter real thresh = 0.6;
    // rise/fall/delay times of PFD output
    parameter real trise = 100p, tfall = 100p, td = 0;

    input REF,FB;
    output UP,DN;

    electrical REF,FB,UP,DN;

    // Internal UP and DN signals
    // * add line here *
    real DN_i,UP_i;
    analog begin

        // Check DN_i state when REF arrives
        // * add line here *
        @(cross(V(REF)-thresh,1))
            if(DN_i < thresh)
                UP_i=VDD;
            else begin
                UP_i = 0;
                DN_i = 0;
            end

        // Check UP_i state when FB arrives
        @(cross(V(FB)-thresh,1))
            // * add line here *
            if(UP_i < thresh)
                DN_i = VDD;
            else begin
```


```


        // * add line here *
        // * add line here *
        UP_i = 0;
        DN_i = 0;
    end

    V(UP) <+ transition(UP_i,td,trise,tfall);
    // * add line here *
    V(DN) <+ transition(DN_i,td,trise,tfall);
end
endmodule


```

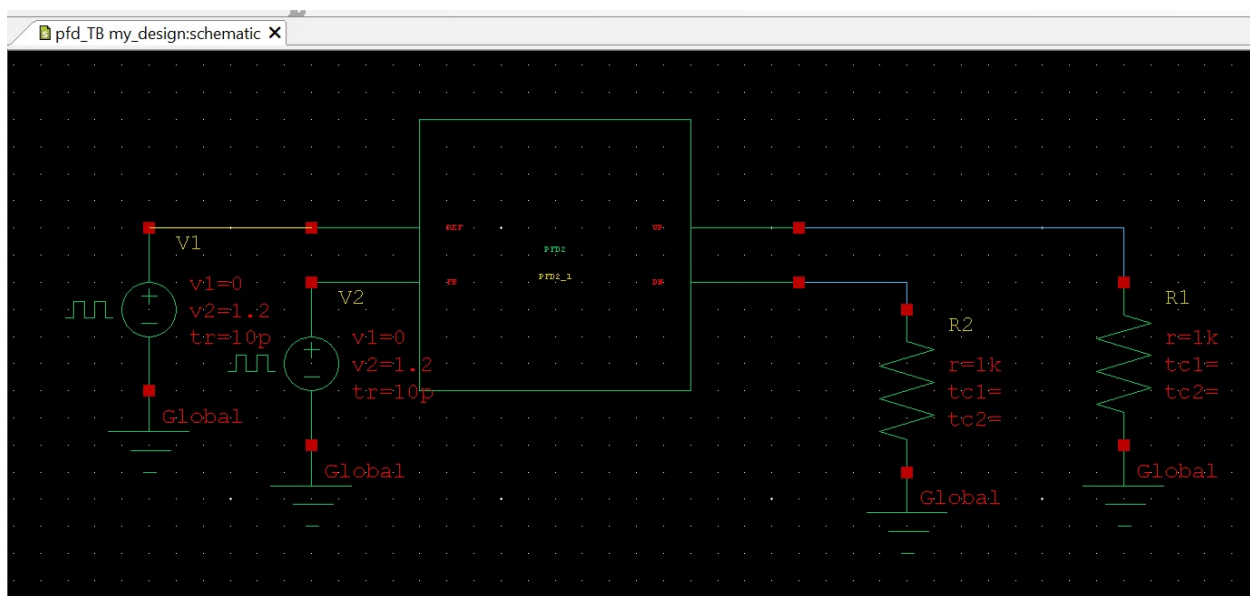2-Make a simple testbench to test the PFD. Deliver a snapshot clearly illustrating the PFD operation (similar to Fig. 6.13 and Fig. 6.14).



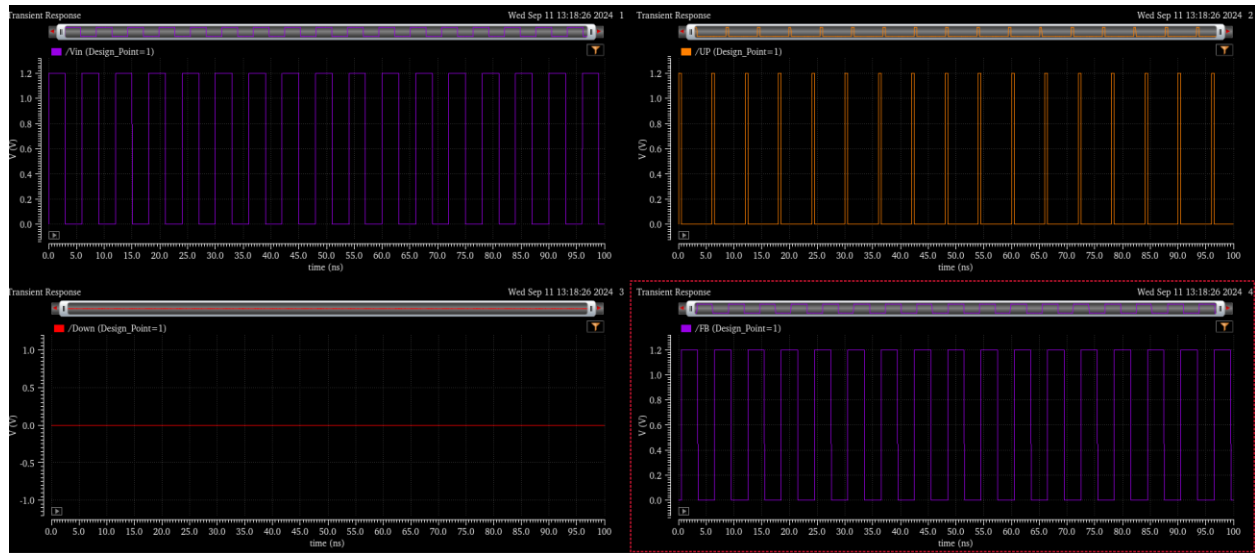

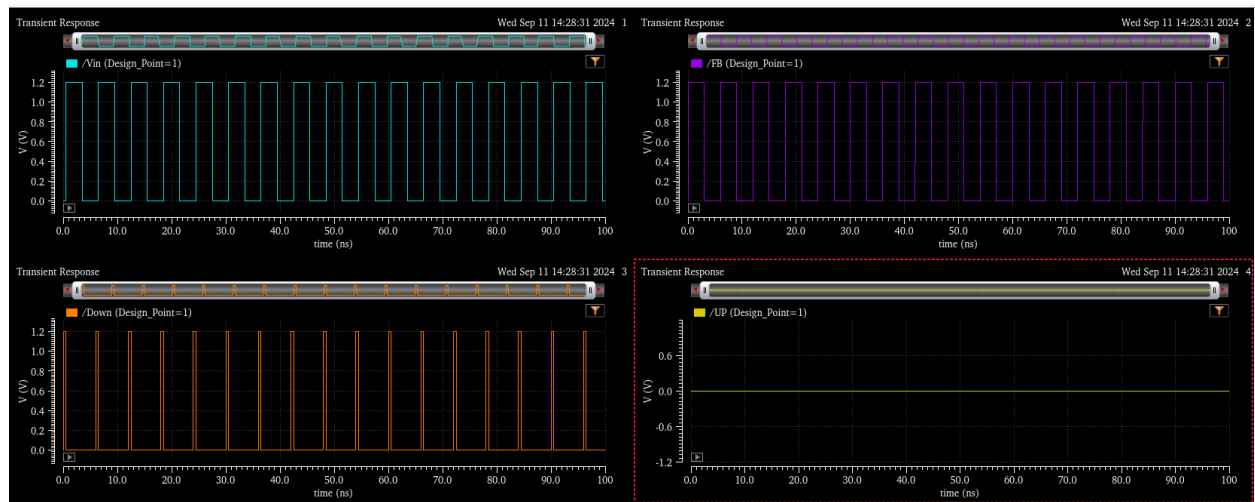The previous figure shows the affect when the V_{in} is faster than the $V_{reference}$ (FB) the UP signal is high



The previous figure shows the affect when the V_{in} is slower than the $V_{reference}$ (FB) the DOWN signal is high

3-Your Verilog-A model for the CHP.

```
`include "constants.vams"
`include "disciplines.vams"

// UP: Up signal
// DN: Dn signal
// IOUT: CHP current output
// Since the output is current, IOUT cannot be left
// unconnected (o.c.) in the testbench
module CHP(UP,DN,IOUT);
    input UP,DN;
    inout IOUT;
    electrical UP,DN,IOUT;

    // ichp: CHP current
    parameter real ichp = 10u from [0:inf);
    // Threshold voltage for digital signals
    parameter real thresh=0.6;
    // rise/fall/delay times of CHP output
    parameter real trise=100p, tfall=100p, td=0;

    // Internal variable for CHP output current
    real IOUT_i = 0;

    analog begin

        // Generate events at UP and DN transitions
        @(cross(V(UP)-thresh,0))
            ;
        // * add line here *
        @(cross(V(DN)-thresh,0))
            ;
        // * add line here *

        if ((V(UP) > thresh) && (V(DN) < thresh))
            IOUT_i = -ichp;
        // * add line here *
        else if ((V(UP) < thresh) && (V(DN) > thresh))
            IOUT_i = ichp;
        else
            // * add line here *
            IOUT_i = 0;
```

```
I(IOUT) <+ transition(IOUT_i,td,trise,tfall);
```

```
end
```

```
endmodule
```


4-Make a simple testbench to test the CHP. Deliver a snapshot clearly illustrating the CHP operation (similar to Fig. 6.18).

190


Lower Limit


Upper Limit

Generate




Clear

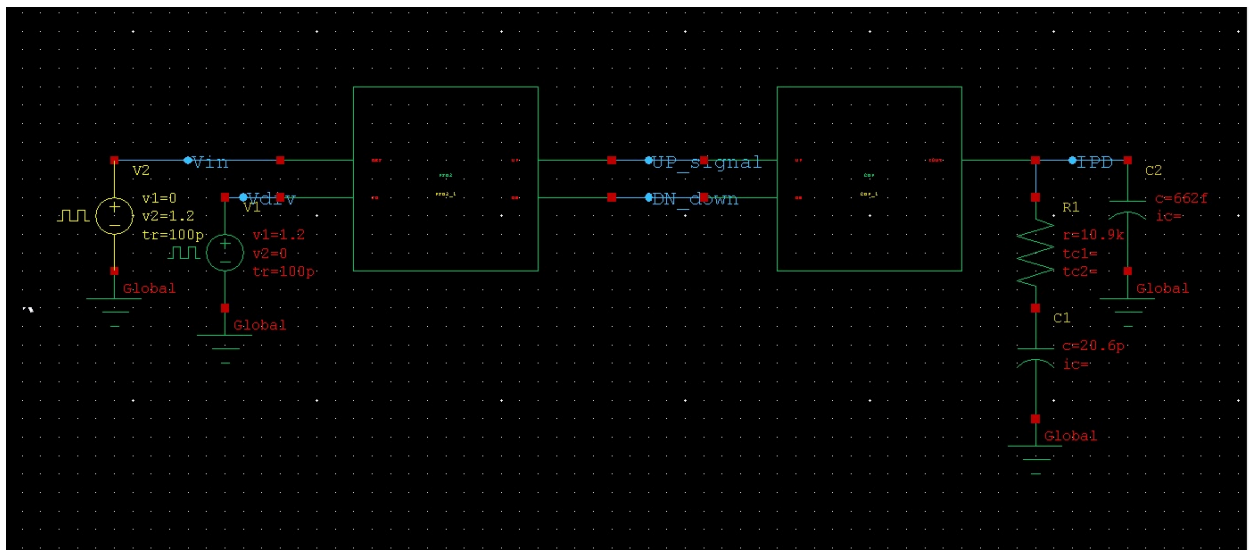

 

 the V_{in} is faster than V_{FB} so the output current for the charge pump is positive



the V_{in} is slower than V_{FB} so the output current for the charge pump is negative

5-Your Verilog-A model for the VCO.

```
// AMS PLL Project: Voltage Controlled Oscillator (VCO)
```

```
`include "constants.vams"
```

```
`include "disciplines.vams"
```

```
module VCO(VCTRL,VOUT);
```

```
    parameter real VHIGH = 1.2;
```

```
    parameter real Vmin=0.2;
```

```
    parameter real Vmax=1 from (Vmin:inf);
```

```
    parameter real Fmin=0.5G from (0:inf);
```

```
    parameter real Fmax=2.02G from (Fmin:inf);
```

```
    parameter real trise=100p, tfall=100p, td=0;
```

```
    input VCTRL;
```

```
    output VOUT;
```

```
    voltage VCTRL,VOUT;
```

```
    // * add line here *
```

```
    real freq,phase,VOUT_i,sine;
```

```
    analog begin
```

```
        // compute the freq from the input voltage
```

```
        freq=((V(VCTRL) - Vmin)*(Fmax - Fmin) / (Vmax - Vmin)) + Fmin;
```

```
        // bound the frequency
```

```
        // * add line here *
```

```
        if (freq > Fmax) freq = Fmax;
```

```
        if (freq < Fmin) freq = Fmin;
```

```
        // calculate the phase (modulo 2*pi)
```

```
        // * add line here *
```

```
        phase=2*`M_PI*idtmod(freq,0.0,1.0,-0.5);
```

```
        // generate the output
```

```
        sine = sin(phase);
```

```
        @(cross(sine,0))
```

```
            ;
```

```
        if (sine > 0)
```



```

        // * add line here *
        VOUT_i=VHIGH;

    else
        // * add line here *
        VOUT_i=0;


    V(VOUT) <+ transition(VOUT_i,td,trise,tfall);


    // bound the time step
    // * add line here *
    $bound_step(0.1/freq);

end
endmodule

```

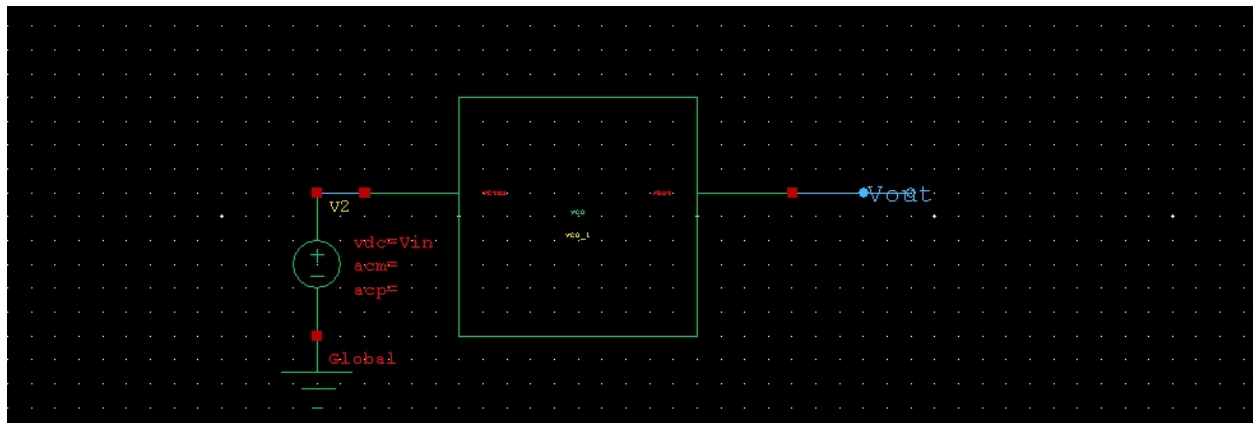6. Make a simple testbench to test the VCO. Deliver a snapshot clearly illustrating the VCO operation (similar to Fig. 6.11, but a single tuning curve is enough, i.e., no corner sim required). Add a marker to show the tuning voltage corresponding to the required output frequency.



 

measure frequency -trace Vout:V -thres

WED 500.03199M

#

625.03953M

#

750.04772M

#

875.05523M

#

1.0000635G

#

1.1250711G

#

1.2500794G

#

1.375087G

#

1.5000953G

window home

7. Your Verilog-A model for the divider.

```
// AMS PLL Project: Frequency Divider

`include "constants.vams"
`include "disciplines.vams"

module divider(VIN,VOUT);

    output VOUT; voltage VOUT;    // output
    input VIN; voltage VIN;       // input (edge triggered)
    parameter real vh=1.2;        // output voltage in high
state
    parameter real vl=0;          // output voltage in low
state
    parameter real vth=0.6; // threshold voltage at input
    parameter integer ratio=8 from [2:inf); // divider
ratio
    parameter real tt=10p from (0:inf); // transition time
of output signal
    parameter real td=0 from [0:inf); // average delay
from input to output

    // *** add line here ***
    real out_value=0,count;

    analog begin


        @(cross(V(VIN) - vth, 1)) begin
            if (count==floor(ratio/2)) begin
                out_value = vh;
                // *** add line here ***
            end
            else if (count==floor(ratio)) begin
                out_value = vl;
                count=0;
                // *** add line here ***

                //else
                //count=count+1;
            end
            count = count + 1;
        end


        V(VOUT) <+ transition(out_value, td, tt);
```

```
end  
endmodule
```

 
8. Make a simple testbench to test the divider. Deliver a snapshot clearly illustrating the divider operation (similar to Fig. 6.20).



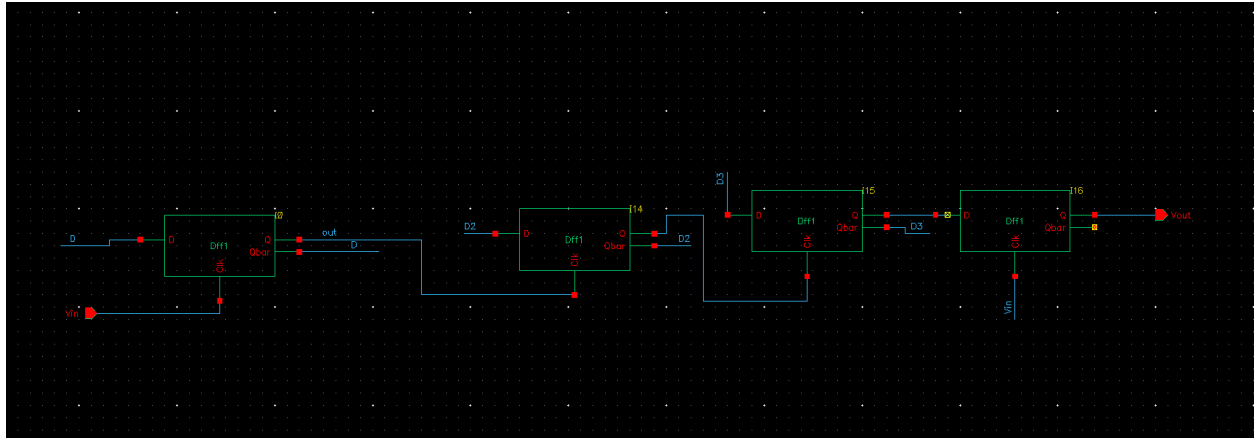
9. Design the divider at the transistor level. Deliver a snapshot clearly illustrating the transistor level schematic of the DFF that you used in the design.



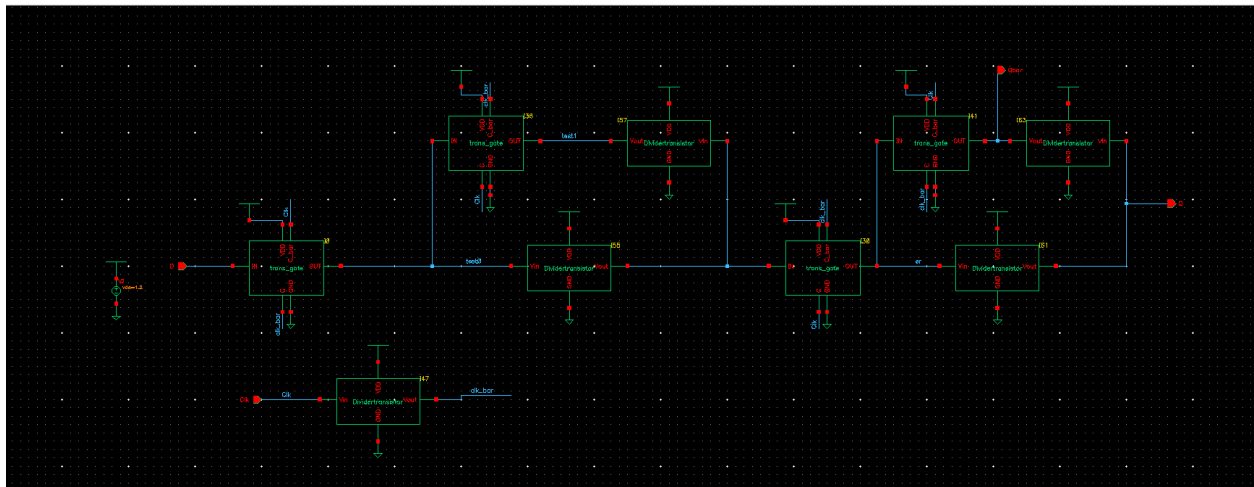
the divider schematic composed of 3 Dff to divide the frequency by 3 and one timing DFF to adjust the output with the clock.



The schematic of DFF

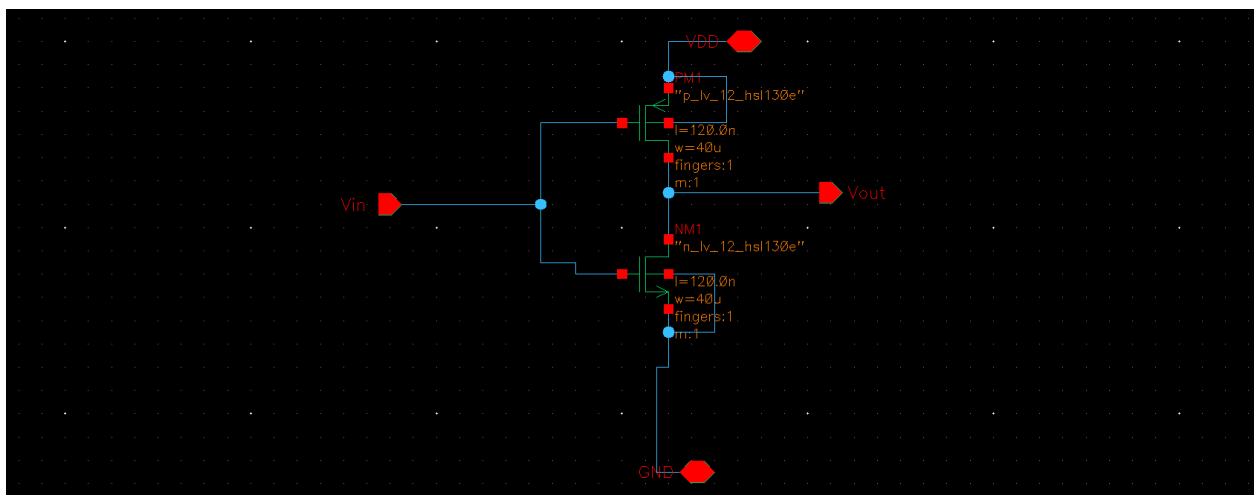


The inverter used in the DFF

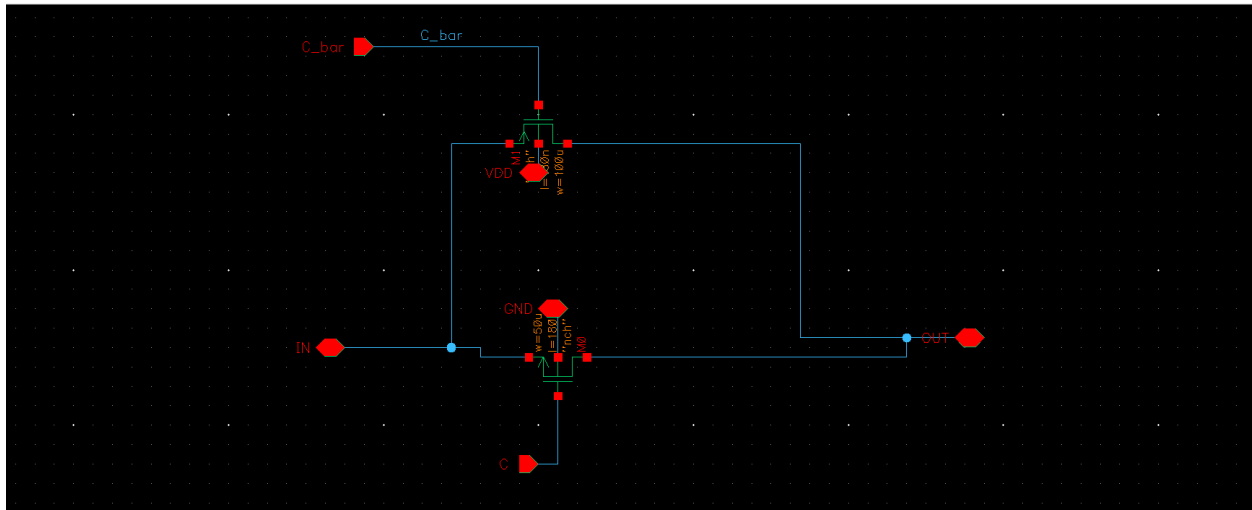


The transmission gate used in the DFF

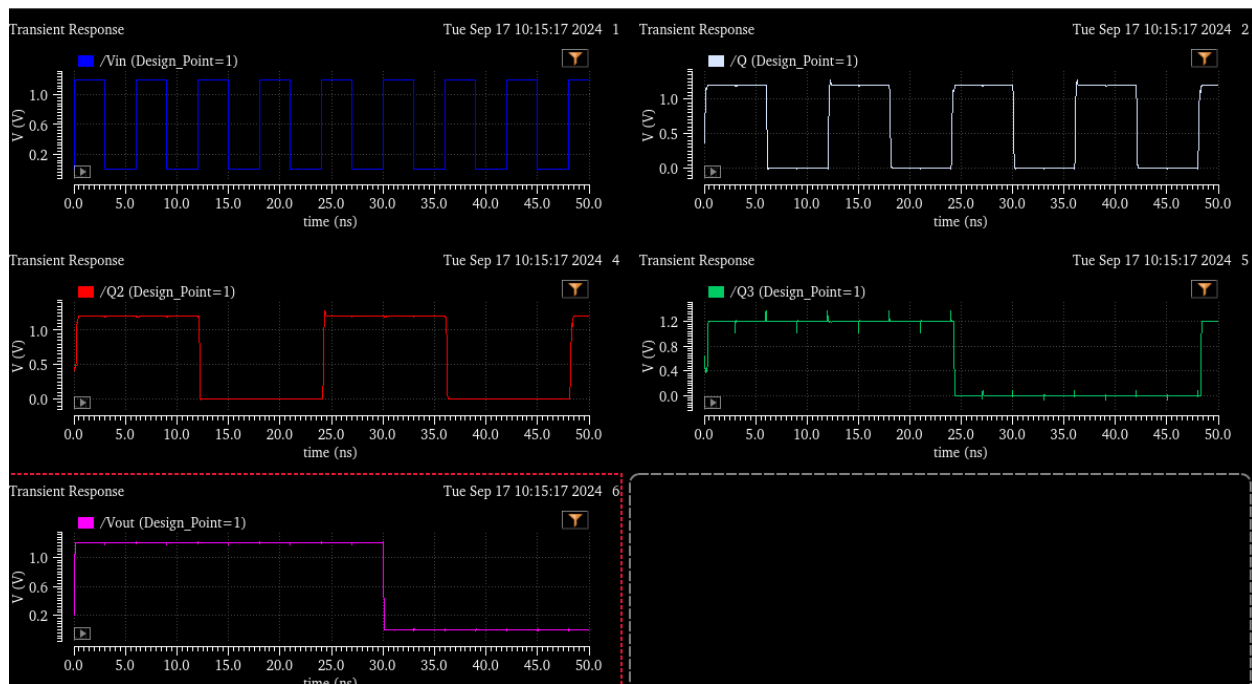10. Using the same previous divider testbench, test your transistor level divider. Deliver a snapshot clearly illustrating the divider operation (similar to Fig. 6.20).



11. Integrate the PLL as shown in Fig. 6.2 using Verilog-A models only. Simulate the PLL using config view and hierarchy editor. Deliver a snapshot clearly illustrating the VCO control voltage (similar to Fig. 6.7). Add a cursor to show the value of the

control voltage after lock.

 

12. Given k_{vco} , analytically calculate the control voltage at which the PLL should achieve lock.


$k_{vco}=1.9\text{GHz}$ and $f_{in}=166.7\text{MHz}$ and $f_{out}=8*166.7\text{MHz}$ & $f_{min}=0.5\text{GHz}$ & $V_{min}=0.2 \rightarrow v_{ctrl}=(f_{out}-f_{min}/k_{vco})+0.2=0.638\text{v}$

13. Compare the control voltage simulated value with the analytically calculated value.

Comment.

They are equal.

 14. Integrate the PLL as shown in Fig. 6.2 using Verilog-A models only. Simulate the PLL using config view and hierarchy editor. Deliver a snapshot clearly illustrating the PLL operation (similar to Fig. 6.8). Add "A/B marker" to indicate the reference and output frequencies.



15. Deliver a snapshot of the log file of the previous simulation clearly illustrating the success of the simulation and the simulation time.


```
Maximum value achieved for any signal of each quantity:
V: V(U) = 1.474 V
I: I(VDD) = 153.3 nA
If your circuit contains signals of the same quantity that are vastly different in size (such as high voltage circuitry combined with low voltage control circuitry), you should consider specifying global option 'bin_reirref=yes'.

-----
Post-Transient Simulation Summary
-----
- To further speed up simulation, consider
  add +raps on command line
-----

During simulation, the CPU load for active processors is :
0 (40.0 %) 1 (41.4 %) 2 (100.0 %) 3 (87.5 %)
Total: 268.9%
Initial condition solution time: CPU = 1.003 ms, elapsed = 899.076 us.
Intrinsic tran analysis time: CPU = 227.983 ms, elapsed = 115.735 ms.
Total time required for tran analysis 'tran': CPU = 233.985 ms, elapsed = 118.734 ms.
Time accumulated: CPU = 674.837 ms, elapsed = 428.345 ms.
Peak resident memory used = 94.6 Mbytes.

Notice from spectre.
32 notices suppressed.

finaltime0: writing operating point information to rawfile.
Opening the PSF file ../psf/finaltime0.info ...
modelParameter: writing model parameter values to rawfile.
Opening the PSF file ../psf/modelParameter.info ...
element: writing instance parameter values to rawfile.
Opening the PSF file ../psf/element.info ...
outputParameter: writing output parameter values to rawfile.
Opening the PSF file ../psf/outputParameter.info ...
designParamVals: writing netlist parameters to rawfile.
Opening the PSFASCII file ../psf/designParamVals.info ...
primitives: writing primitives to rawfile.
Opening the PSFASCII file ../psf/primitives.info.primitives ...
subckits: writing subcircuits to rawfile.
Opening the PSFASCII file ../psf/subckits.info.subckits ...

Aggregate audit (10:14:18 AM, Tue Sep 17, 2024):
Time used: CPU = 757 ms, elapsed = 487 ms, util. = 155%.
Time spent in licensing: elapsed = 25.3 ms, percentage of total = 5.19%.
Peak memory used = 95.4 Mbytes.
Simulation started at: 10:14:17 AM, Tue Sep 17, 2024, with elapsed time (wall clock): 487 ms.
Spectre completes with 0 errors, 13 warnings, and 14 notices.

-----
temp = 27 C
tnom = 27 C
tempEffects = all
errpreset = moderate
method = trapezoid
iteration = 3.5
reirref = sigisobal
cmn = 0 F
gmtn = 1 pS
rabshort = 1 nHm

Notice from spectre during transient analysis 'tran'.
Multithreading is disabled due to the size of the design being too small.

Output and IChodeset summary:
save 2 (current)
save 30 (voltage)

tran: time = 1.271 ms (2.54 %), step = 277.3 ps (555 nH)

Notice from spectre at time = 1.82534 ns during transient analysis 'tran'.
Found trapezoidal ringing on node V0-p.
Notice from spectre at time = 2.4797 ns during transient analysis 'tran'.
Found trapezoidal ringing on node V0-p.
Notice from spectre at time = 3.01 ns during transient analysis 'tran'.
Found trapezoidal ringing on node V0-p.


tran: time = 4.124 ms (8.25 %), step = 381.4 ps (763 nH)

Notice from spectre at time = 4.88638 ns during transient analysis 'tran'.
Found trapezoidal ringing on node V0-p.
Notice from spectre at time = 5.48319 ns during transient analysis 'tran'.
Found trapezoidal ringing on node V0-p.
Further occurrences of this notice will be suppressed.

tran: time = 6.252 ns (12.5 %), step = 3.468 ps (6.94 nH)
tran: time = 9.01 ns (18 %), step = 748.7 ps (1.5 %)
tran: time = 12 ns (24 %), step = 765.6 ps (1.53 %)
tran: time = 13.93 ns (27.8 %), step = 634.4 ps (1.27 %)
tran: time = 16.59 ns (33.2 %), step = 627.5 ps (1.25 %)
tran: time = 18.8 ns (37.6 %), step = 130 ps (260 nH)
tran: time = 21.27 ns (42.5 %), step = 31.1 ps (66.2 nH)
tran: time = 24 ns (48 %), step = 711.2 ps (1.42 %)
tran: time = 27.01 ns (54 %), step = 829.7 ps (1.66 %)
tran: time = 29.19 ns (58.4 %), step = 809.5 ps (1.62 %)
tran: time = 31.48 ns (63 %), step = 480.9 ps (962 nH)
tran: time = 33.89 ns (67.7 %), step = 169.8 ps (340 nH)
tran: time = 36.26 ns (72.5 %), step = 9.707 ps (19.4 nH)
tran: time = 39.01 ns (78 %), step = 541.7 ps (1.08 %)
tran: time = 41.29 ns (82.6 %), step = 709.3 ps (1.42 %)
tran: time = 44.28 ns (88.6 %), step = 764.4 ps (1.53 %)
tran: time = 46.56 ns (93.1 %), step = 453 ps (906 nH)
tran: time = 48.86 ns (97.7 %), step = 136.4 ps (273 nH)
```

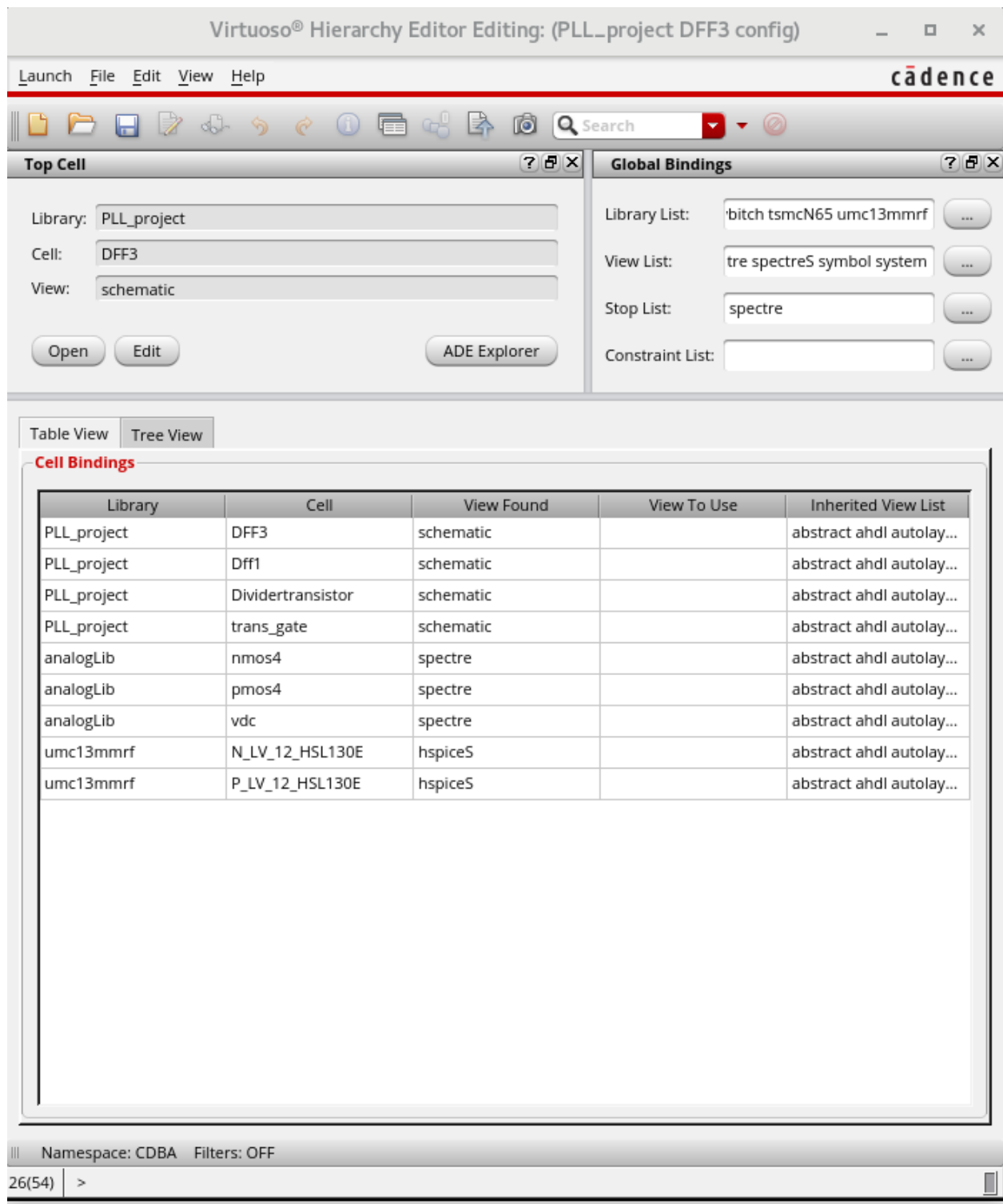16. Replace the Verilog-A view of the divider with the schematic (transistor level) view.


Deliver a snapshot of the new configuration in hierarchy editor.




Config view

 17. Integrate the PLL as shown in Fig. 6.2 using Verilog-A models of all blocks except the divider. Use the schematic view of the divider. Simulate the PLL using config view

and hierarchy editor. Deliver a snapshot clearly illustrating the VCO control voltage (similar to Fig. 6.23).



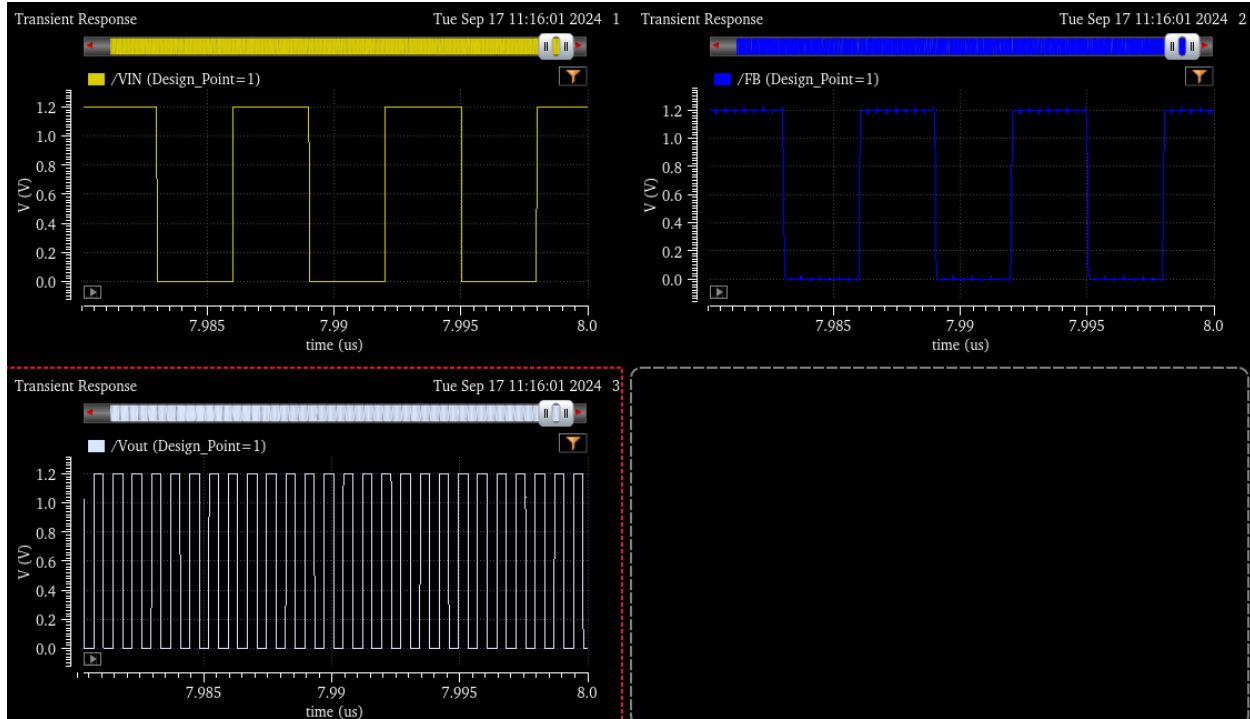18. Integrate the PLL as shown in Fig. 6.2 using Verilog-A models of all blocks except the divider. Use the schematic view of the divider. Simulate the PLL using config view and hierarchy editor. Deliver a snapshot clearly illustrating the PLL operation (similar to Fig. 6.24). Add “A/B marker” to indicate the reference and output frequencies.



19. Deliver a snapshot of the log file of the previous simulation clearly illustrating the success of the simulation and the simulation time.

```

Notice from spectre during 'transient analysis' 'tran'.
  Trapezoidal ringing is detected during tran analysis.
  Please use methodtrap for better results and performance.

Maximum value achieved for any signal of each quantity:
V: V(I22_O) = 1.492 V
I: I(I1F_VOUT_Flow) = 266.3 nA
If your circuit contains signals of the same quantity that are vastly different in size (such as high voltage circuitry combined with low voltage control circuitry), you should consider specifying global option 'bin_refref=yes'.

-----
Post-Transient Simulation Summary
-----
- To further speed up simulation, consider
  add +aps on command line
-----

During simulation, the CPU load for active processors is :
0 (27.8 %) 1 (33.9 %) 2 (19.6 %) 3 (11.5 %)
Total: 92.8%
Initial condition solution time: CPU = 917 us, elapsed = 984.907 us.
Intrinsic tran analysis time: CPU = 163.093 s, elapsed = 163.018 s.
Total time required for 'tran analysis' 'tran': CPU = 163.165 s (2m 43.1s), elapsed = 163.088 s (2m 43.1s).
Time accumulated: CPU = 163.789 s (2m 43.8s), elapsed = 163.578 s (2m 43.6s).
Peak resident memory used = 357 Mbytes.

finalTimeOP: writing operating point information to rawfile.
Opening the PSF file ../psf/finalTimeOP.info ...
ModelParameter: writing model parameter values to rawfile.
Opening the PSF file ../psf/modelParameter.info ...
element: writing instance parameter values to rawfile.
Opening the PSF file ../psf/element.info ...
outputParameter: writing output parameter values to rawfile.
Opening the PSF file ../psf/outputParameter.info ...
designParamVals: writing netlist parameters to rawfile.
Opening the PSF file ../psf/designParamVals.info ...
primitives: writing primitives to rawfile.
Opening the PSF file ../psf/primitives.info.primitives ...
subckts: writing subcircuits to rawfile.
Opening the PSF file ../psf/subckts.info.subckts ...

Aggregate audit (11:15:59 AM, Tue Sep 17, 2024):
Time used: CPU = 164 s (2m 43.9s), elapsed = 164 s (2m 43.8s), util. = 100%.
Time spent in licensing: elapsed = 24.8 ms.
Peak memory used = 362 Mbytes.
Simulation started at: 11:13:15 AM, Tue Sep 17, 2024, ended at: 11:15:59 AM, Tue Sep 17, 2024, with elapsed time (wall clock): 164 s (2m 43.8s).
spectre completes with 0 errors, 13 warnings, and 11 notices.

```

20. Compare the simulation time of (13) and (17). Comment.

Simulation time of Verilog A model is: 757ms

Simulation time of transistor level model is: 164s

The time taken by transistor level model is much higher .