
EE230-02 RFIC II

Fall 2018

Lecture 16: Phase-Locked Loops


Prof. Sang-Soo Lee
sang-soo.lee@sjsu.edu
ENG-259

How Are PLL's used?

- Frequency Synthesis (e.g. generating a 1 GHz clock from a 100 MHz reference in a CPU)



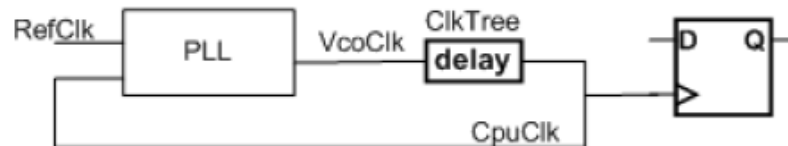
- Skew Cancellation (e.g. phase-aligning an internal clock to the I/O clock) (May use a DLL instead)



How Are PLL's used?

Ser des

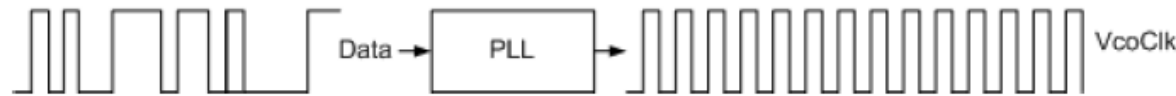- Extracting a clock from a random data stream (e.g. serial-link clock-data recovery) ~~///~~




- Reference Clean-Up (e.g. low-pass filter source-synchronous clock in high-speed I/O)



↑ over many HFC & LAF will clean it

What is a PLL?

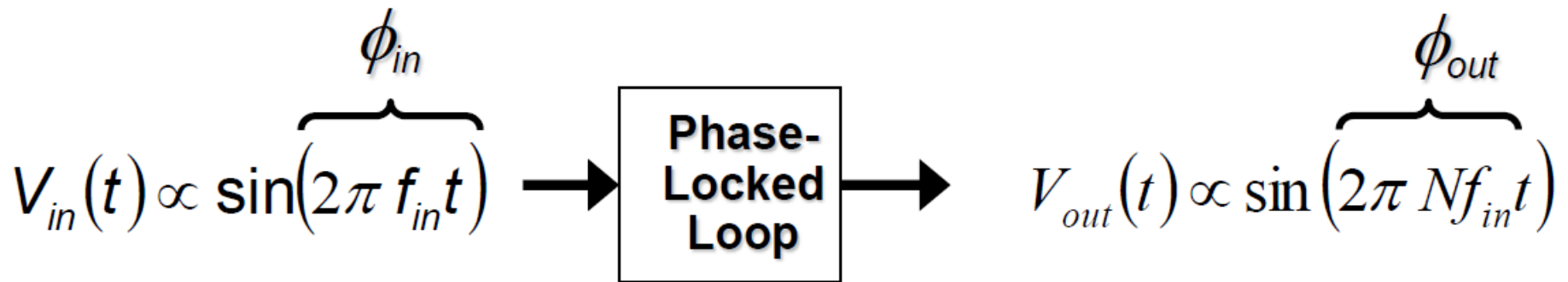- Negative feedback control system where f_{out} tracks f_{in} and rising edges of input clock align to rising edges of output clock
- Mathematical model of frequency synthesizer





- **Phase = \int frequency**

$$\phi(t) = 2\pi \int f(t) dt \leftrightarrow f(t) = \frac{1}{2\pi} \frac{d\phi(t)}{dt}$$


- **When phase-locked,** $\phi_{out} = N\phi_{in} \rightarrow f_{out} = Nf_{in}$

What does PLL Bandwidth means?

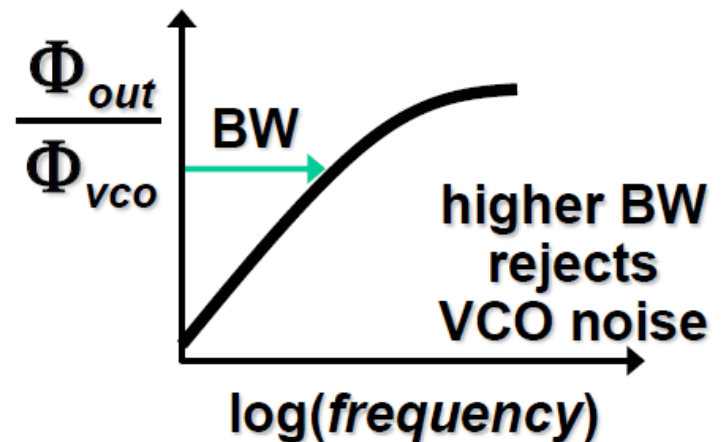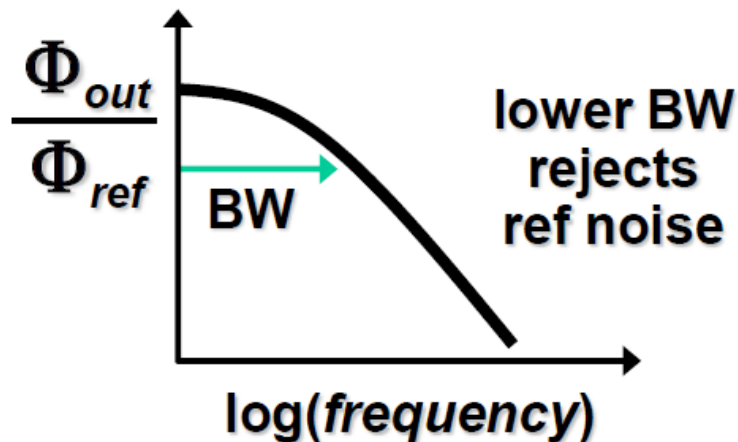- PLL acts as a low-pass filter with respect to the reference modulation. High-frequency reference jitter is rejected
- Low-frequency reference modulation (e.g., spread-spectrum clocking) is passed to the VCO clock
- PLL acts as a high-pass filter with respect to VCO jitter
- “Bandwidth” is the modulation frequency at which the PLL begins to lose lock with the changing reference (-3dB)





Simple Type-I PLL and Loop Filter

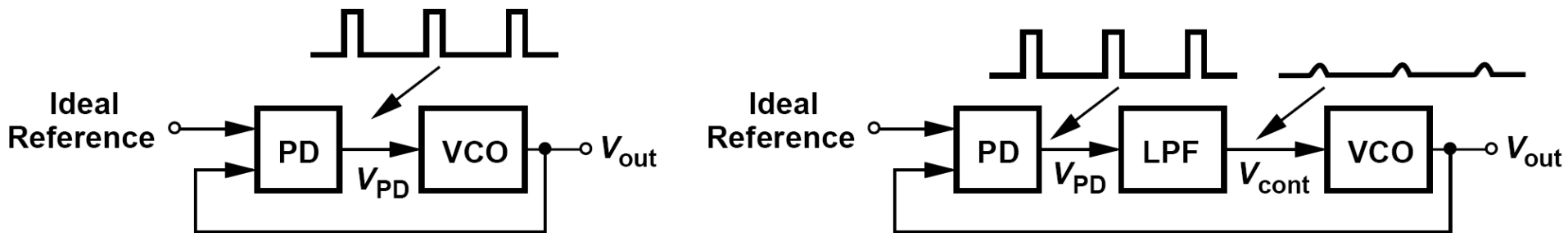

- Negative feedback loop: if the “loop gain” is sufficiently high, the circuit minimizes the input error. *Phase error but Type I have stability problems*
- The PD produces repetitive pulses at its output, modulating the VCO frequency and generating large sidebands.
- Insert a low-pass filter between the PD and the VCO to suppress these pulses. \Rightarrow Smooth the signals

Simple PLL: Phase Locking

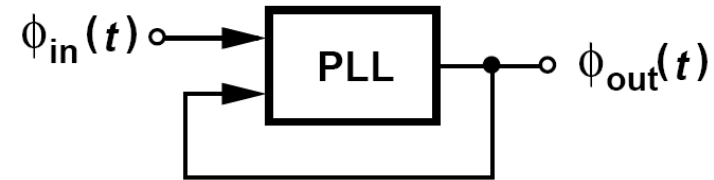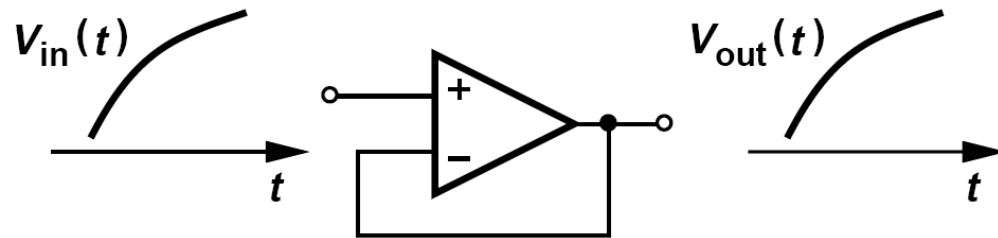



$$\phi_{out}(t) - \phi_{in}(t) = \text{constant}$$

$$\frac{d\phi_{out}}{dt} = \frac{d\phi_{in}}{dt}$$

- Loop is “locked” if $\phi_{out}(t) - \phi_{in}(t)$ is constant with time.
- Phase locking makes the input and output frequencies of the PLL exactly equal.

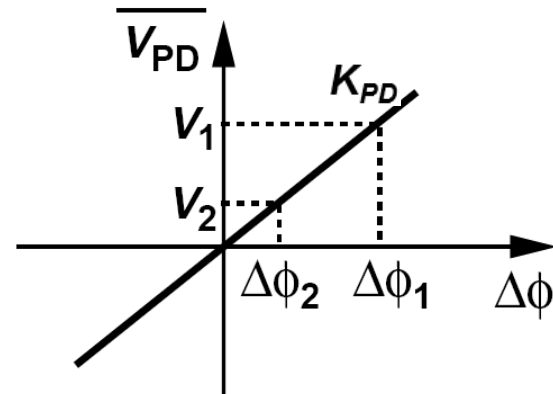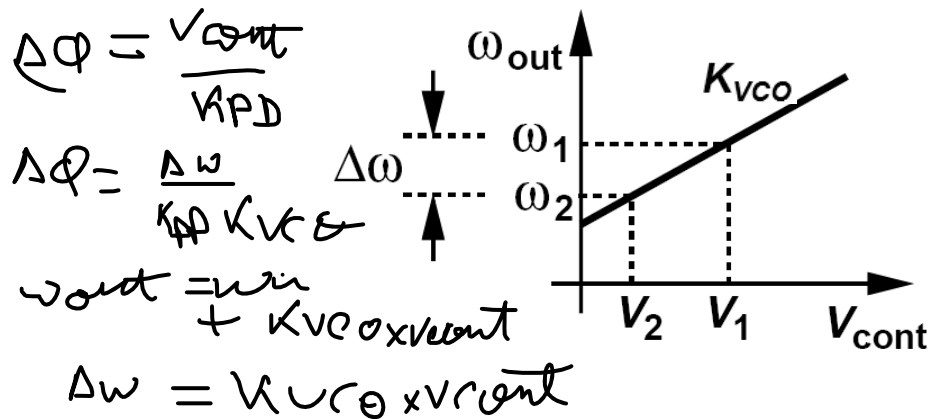Example of Phase Error



If the input frequency changes by $\Delta\omega$, how much is the change in the phase error?
Assume the loop remains locked.



$$V_{cont} \text{ change} = \Delta\omega / K_{VCO} \quad \longrightarrow \quad \Delta\phi_2 - \Delta\phi_1 = \frac{\Delta\omega}{K_{PD} K_{VCO}}$$


- Phase error varies with the frequency.
- To minimize this variation, $K_{PD} K_{VCO}$ must be maximized.
- $K_{PD} K_{VCO}$ is called the “loop gain”.

Response of PLL to Input Frequency Step

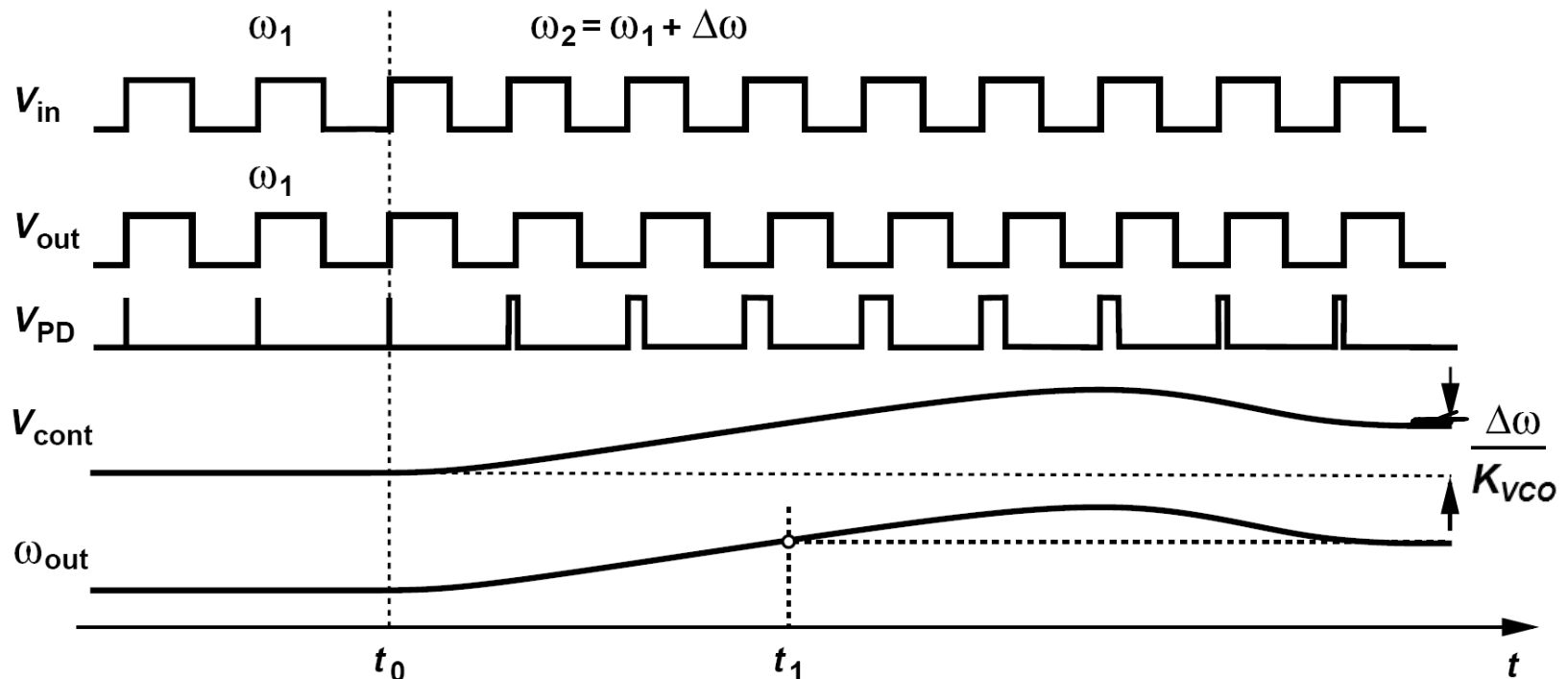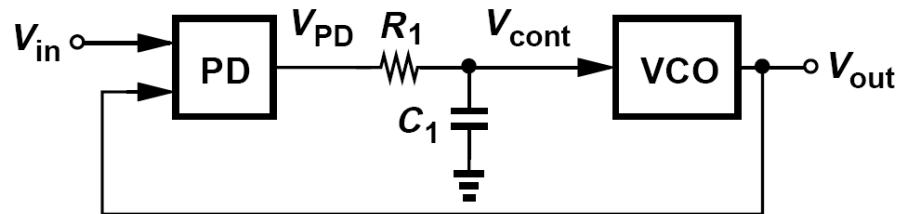

- The loop locks only after two conditions are satisfied:
- (1) ω_{out} becomes equal to ω_{in}
 - (2) the difference between ϕ_{in} and ϕ_{out} settles to its proper value

Loop Dynamics: Phase Domain Model

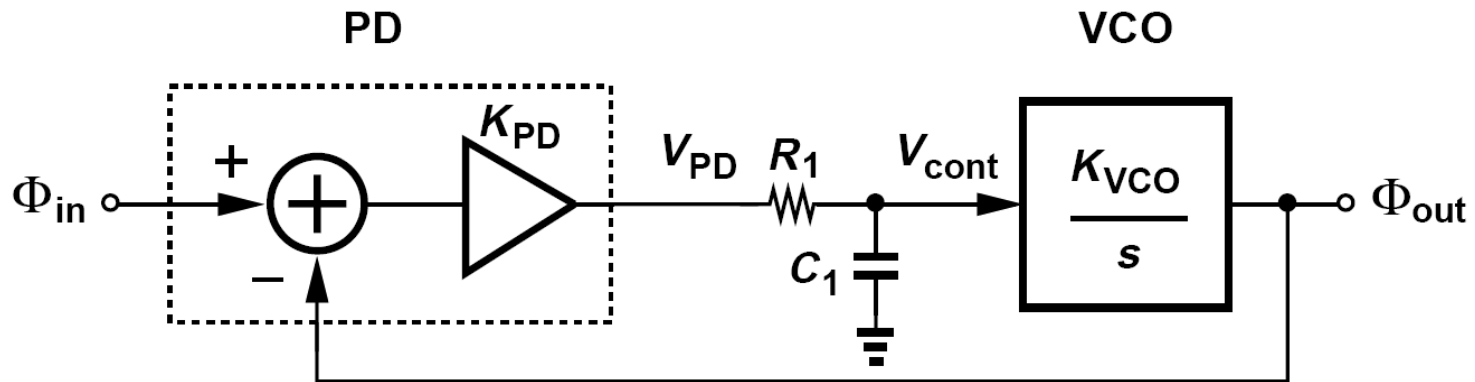

Open-loop transfer function

$$[K_{PD}/(R_1C_1s + 1)](K_{VCO}/s)$$

Closed-loop transfer function

$$H(s) = \frac{\phi_{out}}{\phi_{in}}(s) = \frac{K_{PD}K_{VCO}}{R_1C_1s^2 + s + K_{PD}K_{VCO}}.$$

Damping Factor and Natural Frequency

$$H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}}{K_{PD}K_{VCO}}}$$

$$\omega_n = \sqrt{K_{PD}K_{VCO}\omega_{LPF}}$$


ζ is inversely proportional to K_{VCO} .

Behavior of the open-loop transfer function, H_{open} , for two different values of K_{VCO}

As K_{VCO} increases, the unity-gain frequency rises, thus reducing the phase margin (PM).

➤ The damping factor is typically chosen to be $\sqrt{2}/2$ or larger so as to provide a well-behaved (critical damped or overdamped) response.


➤ $\omega_{LPF} = 1/(R_1C_1)$

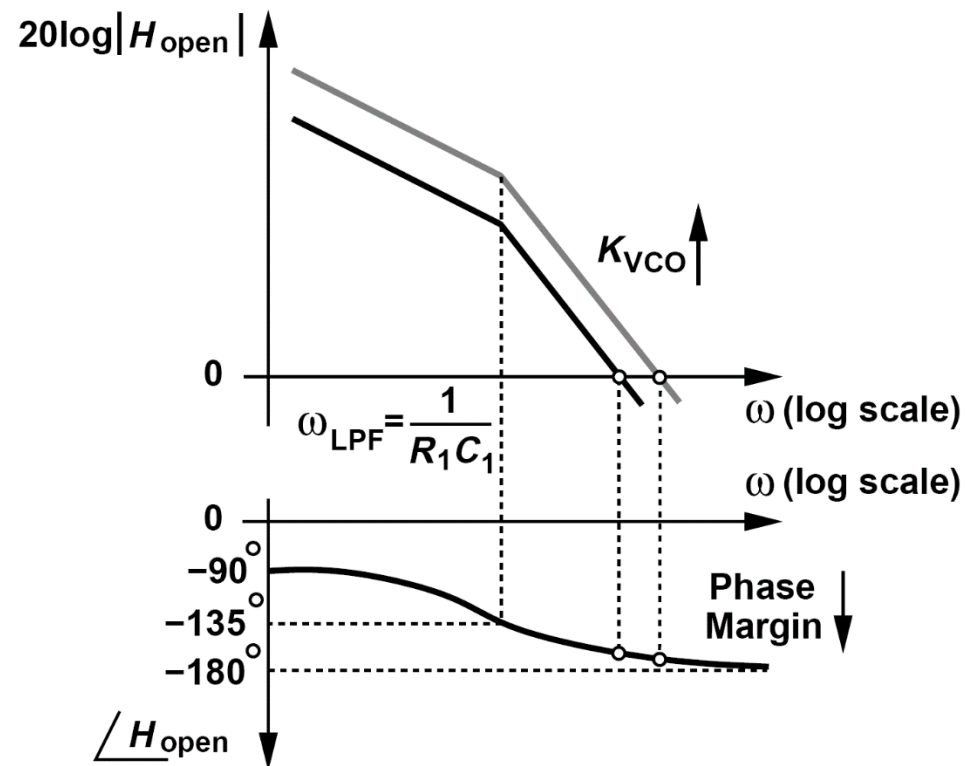




Drawbacks of Type-I PLL

- Tight relation between the loop stability and the corner frequency of the low-pass filter. Ripple on the control line modulates the VCO frequency and must be suppressed by choosing a low value for ω_{LPF} , leading to a less stable loop

$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}}{K_{PD} K_{VCO}}}$$


- Suffers from a limited “acquisition range” \Rightarrow 
If the VCO frequency and the input frequency are very different at the start-up, the loop may never “acquire” lock.

Type-II PLLs: Phase/Frequency Detectors

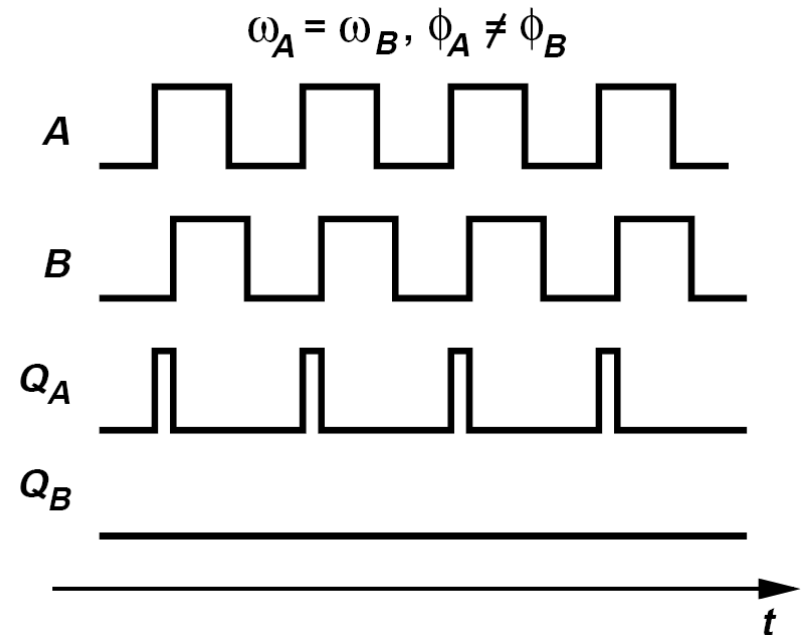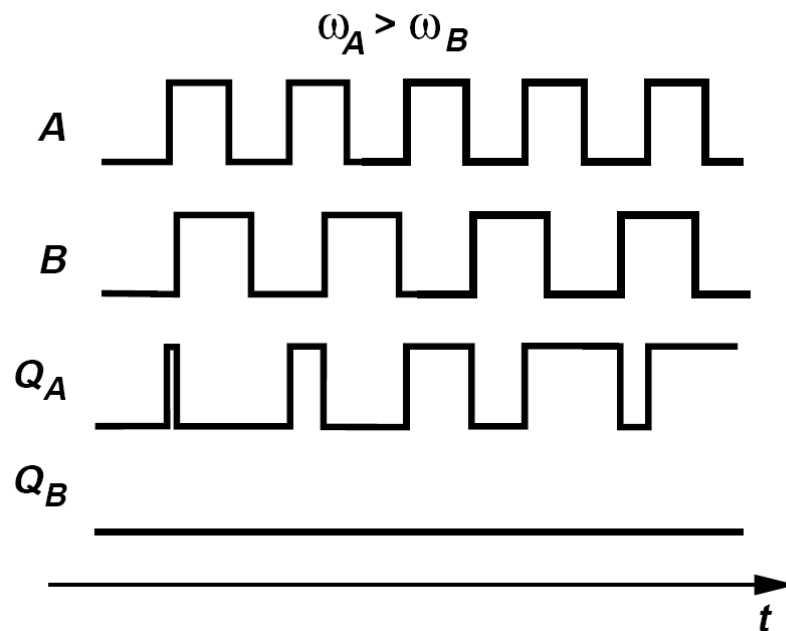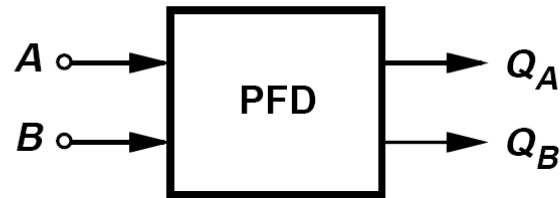

- A rising edge on A yields a rising edge on Q_A (if Q_A is low)
- A rising edge on B resets Q_A (if Q_A is high)
- The circuit is symmetric with respect to A and B (and Q_A and Q_B)

PFD: Logical Implementation

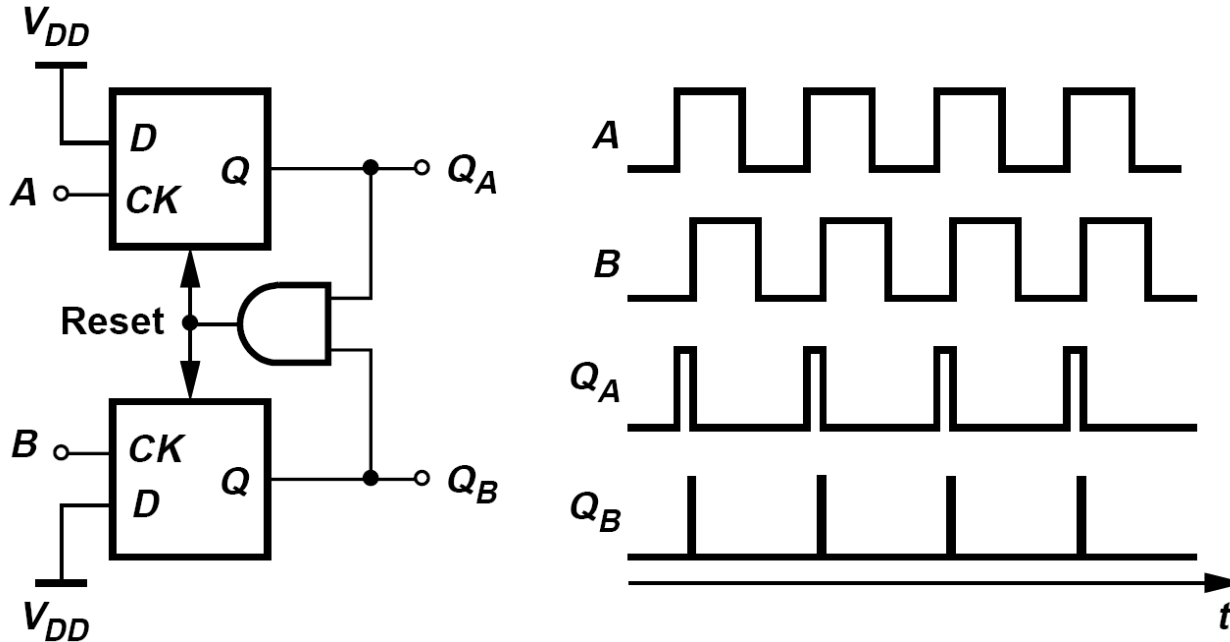

- Q_A and Q_B are simultaneously high for a duration given by the total delay through the AND gate and the reset path of the flipflops.